




HARDWARE FELLOWSHIP 2023

DAY 4

INSTRUCTOR: SUSHANT PANDEY



A decorative network diagram in the top-left corner, featuring a cluster of interconnected nodes. Some nodes are represented by solid grey circles, while others are larger circles with concentric rings. These nodes are connected by thin, light-grey lines, some of which are solid and others dashed, creating a web-like structure.

WIRELESS COMMUNICATION


A decorative network diagram in the bottom-right corner, similar to the one in the top-left. It shows a cluster of interconnected nodes, including solid grey circles and larger concentric-ring circles, connected by thin, light-grey lines (some solid, some dashed).



Encoder Logic




Decoder Logic

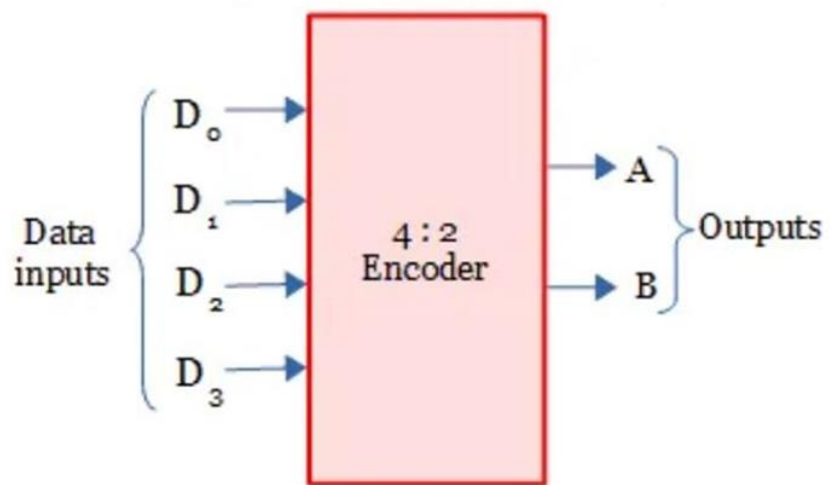

Inputs				Output	
D_3	D_2	D_1	D_0	B	A
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

4-bit binary encoder

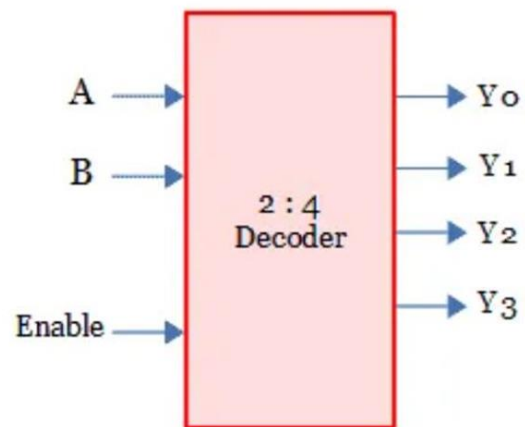

Inputs			Outputs			
EN	A	B	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0




Receiver

Antennas are electrical devices that transform the electrical signals to radio signals in the form of Electromagnetic (EM) Waves and vice versa. These Electromagnetic Waves propagates through space.





Transmitter


WIRELESS COMMUNICATION

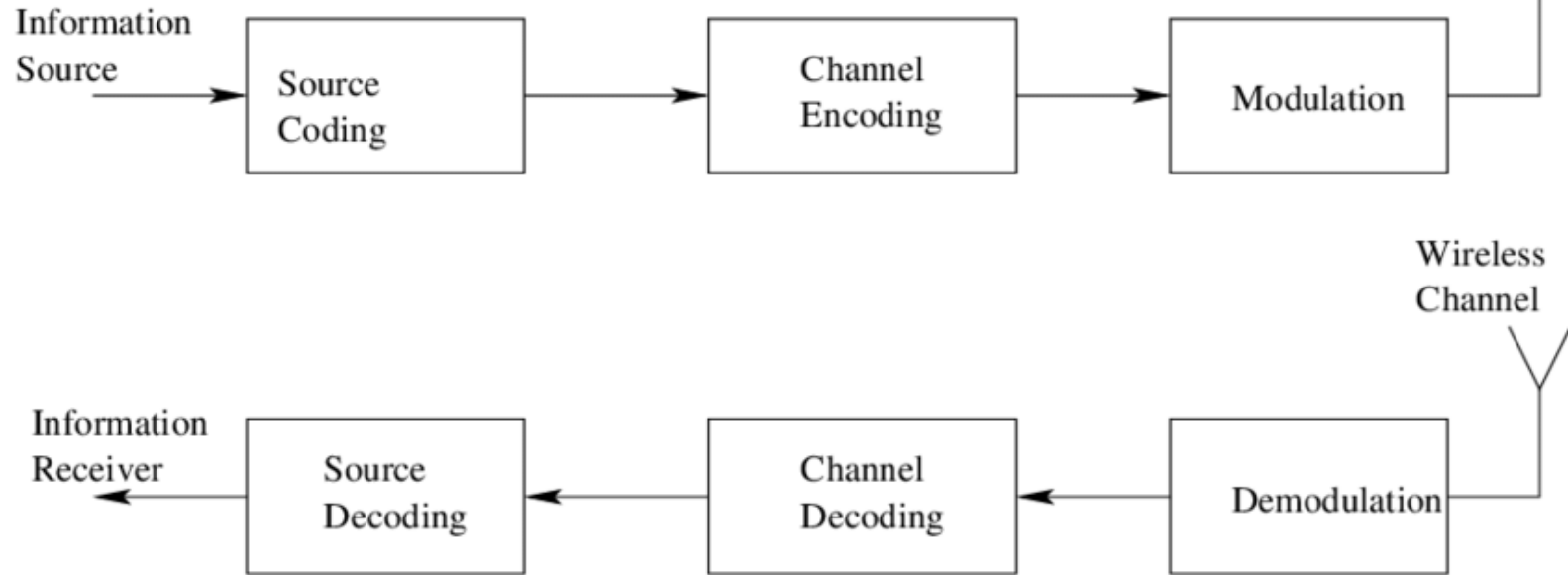

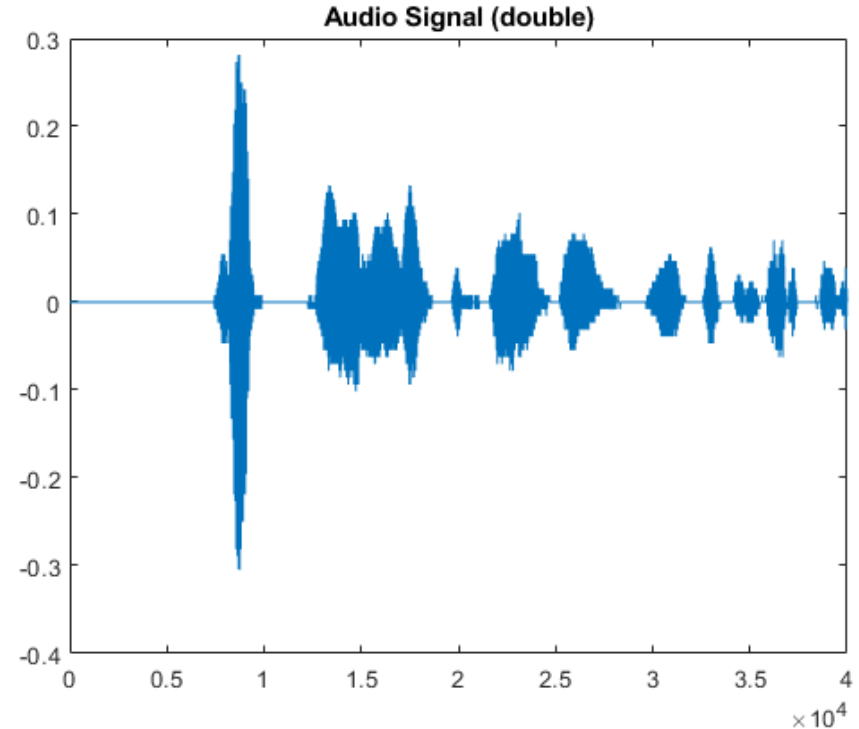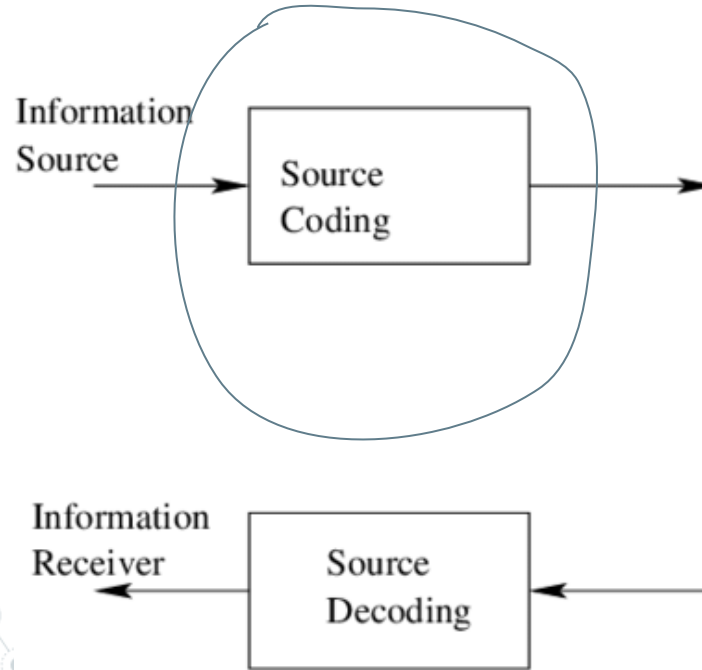Source encoding **aims to convert information waveforms (text, audio, image, video, etc.)** in to a suitable form for applying signal processing techniques.
(Remove redundant information)



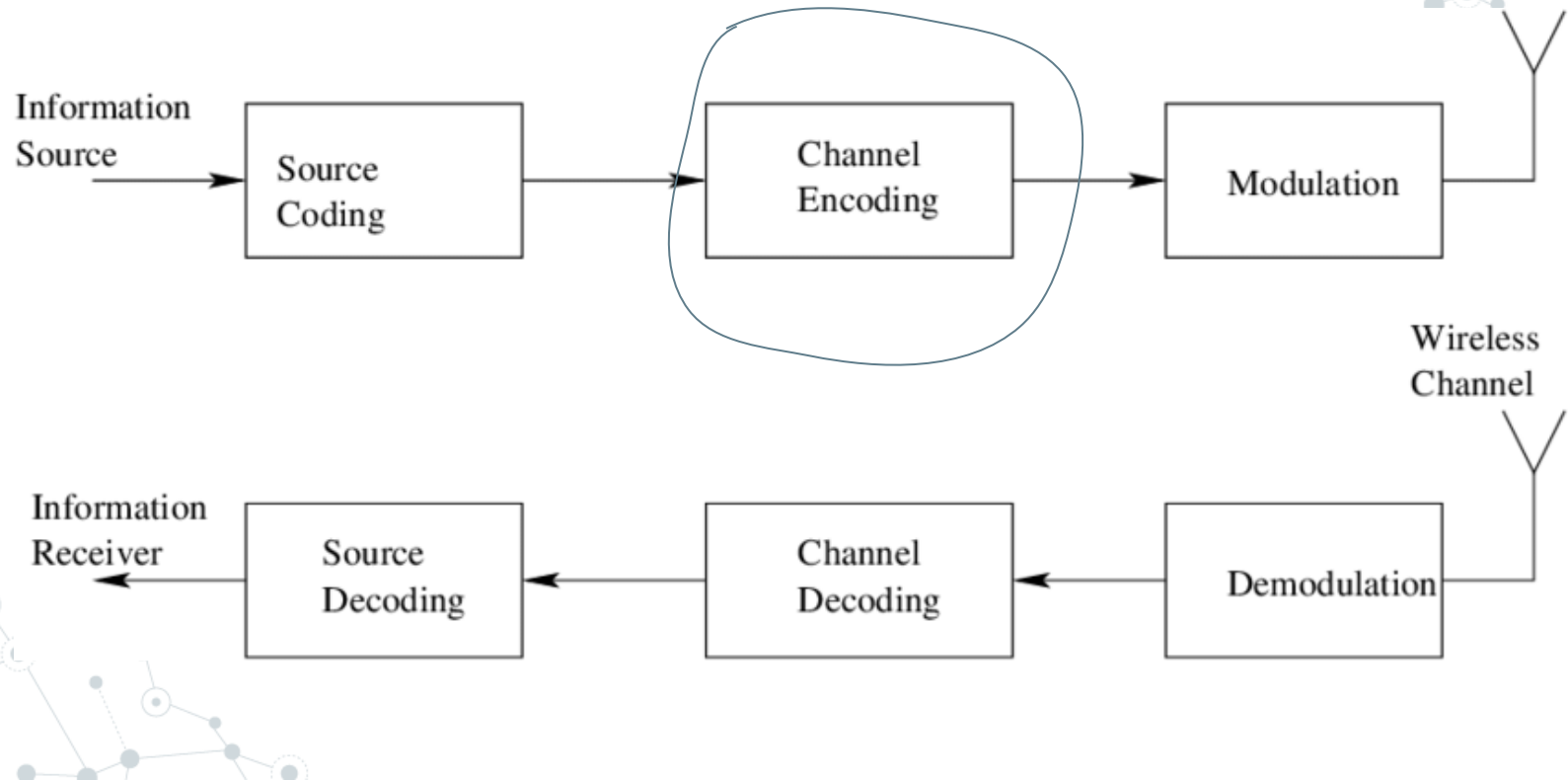
The channel encoder, **does the coding for error correction**. During the transmission of the signal, due to the noise in the channel, the signal may get altered and hence to avoid this, the channel encoder adds some redundancy.





Modulation is **the process of converting data into radio waves by adding information to an electronic or optical carrier signal.**

(process of encoding information from a message source in a way that is suitable for transmission)

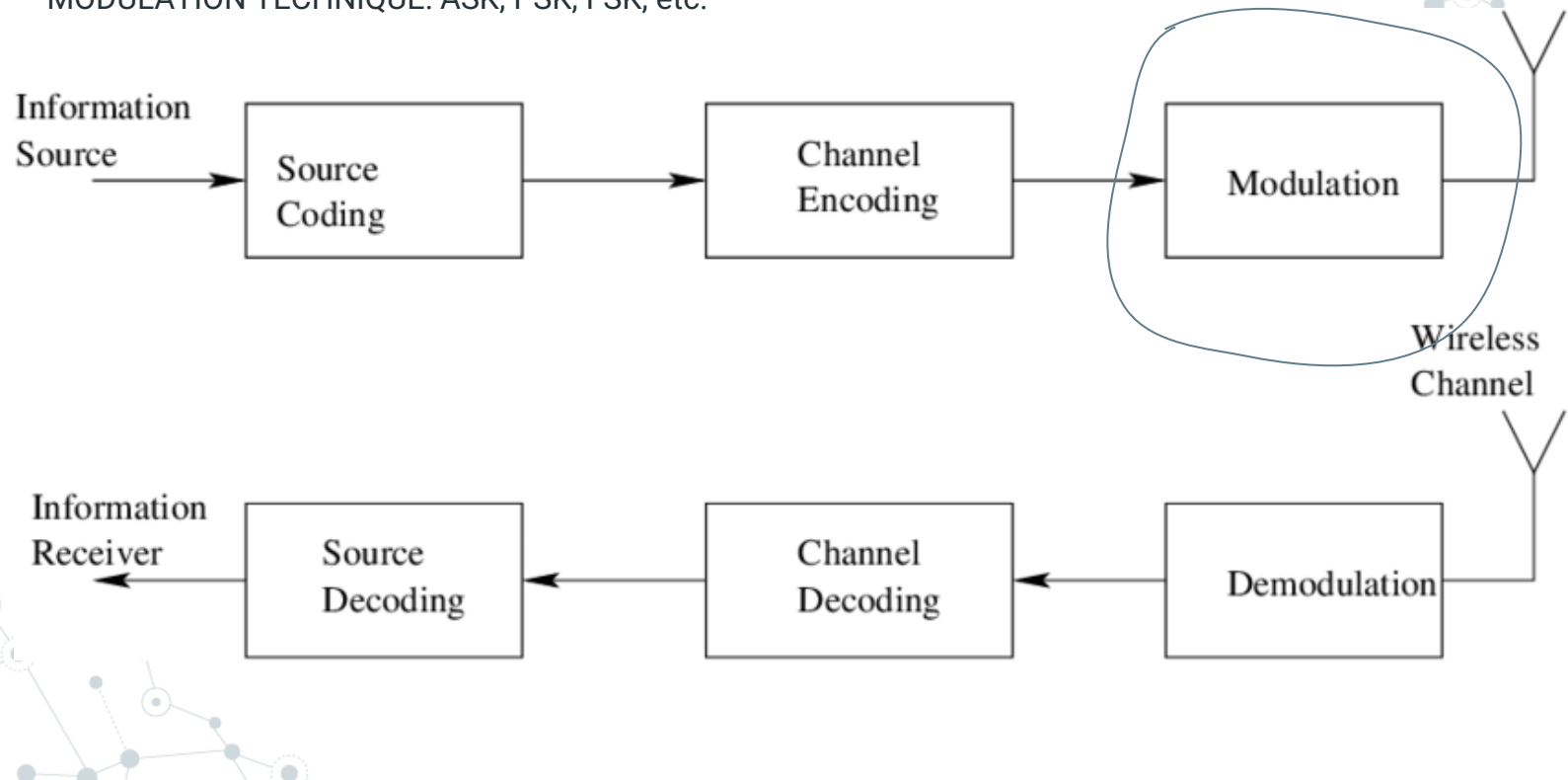
MODULATION TECHNIQUE: ASK, PSK, FSK, etc.



ASK (Amplitude Shift Keying (Modulation)

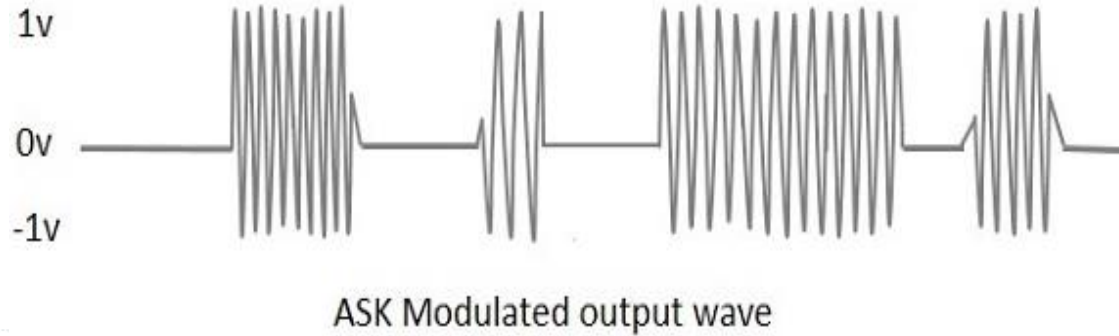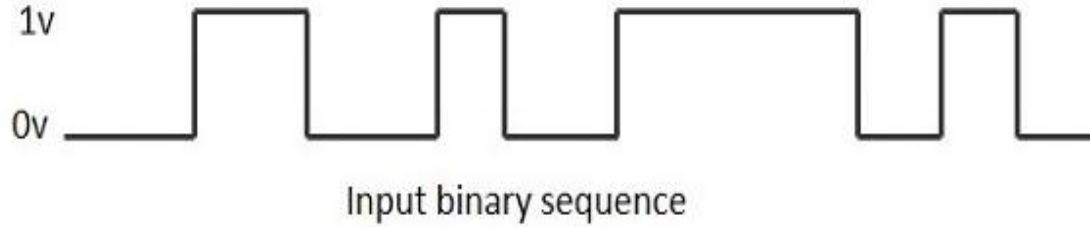

ASK (Amplitude Shift Keying (Modulation)

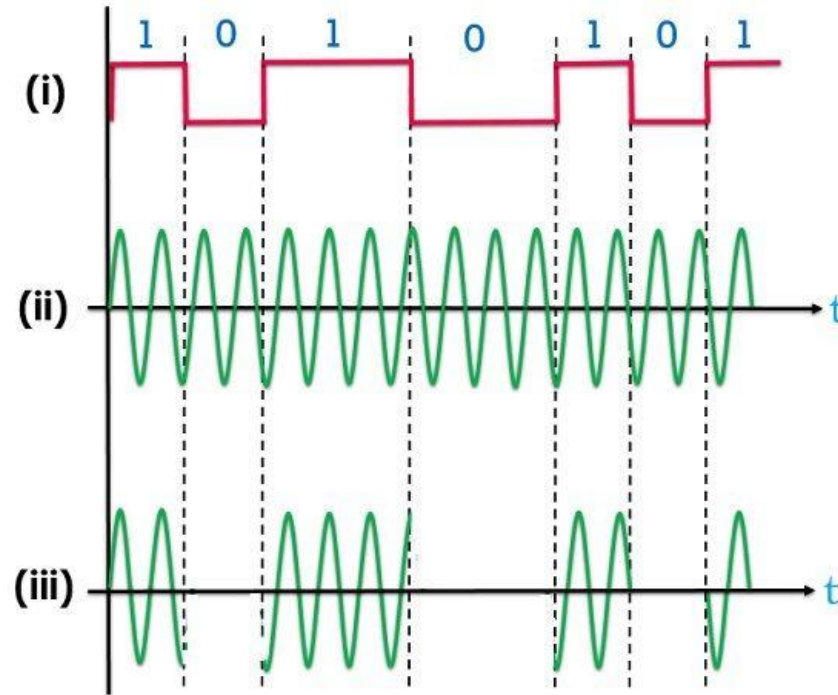

(i) = Digital bit sequence


(ii) = Carrier wave

(iii) = ASK modulated wave

Generation of ASK




Generation of ASK signal

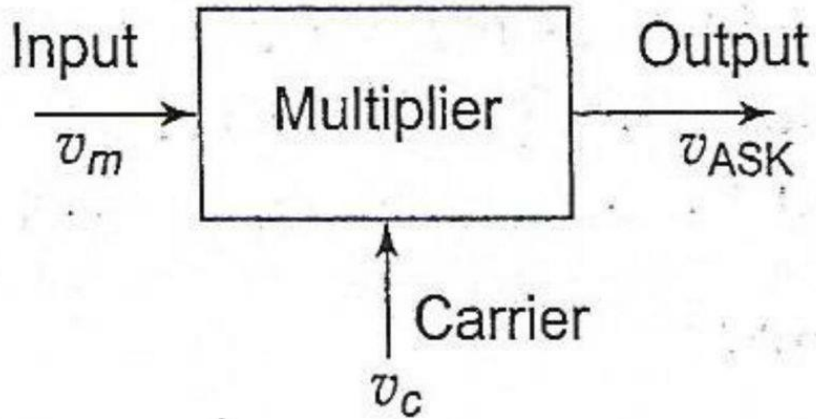


Block diagram of generation of ASK

Multiplier

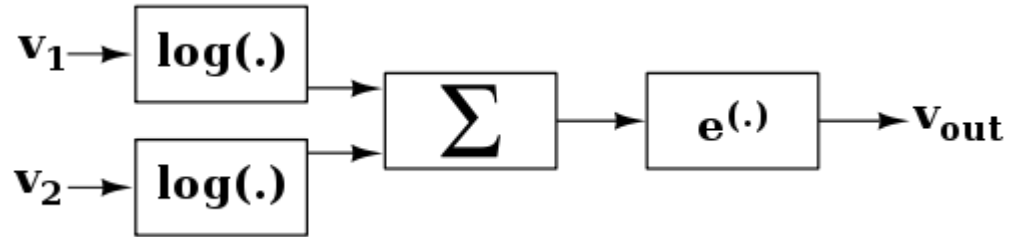


$$\log(xy) = \log(x) + \log(y)$$

Op amp

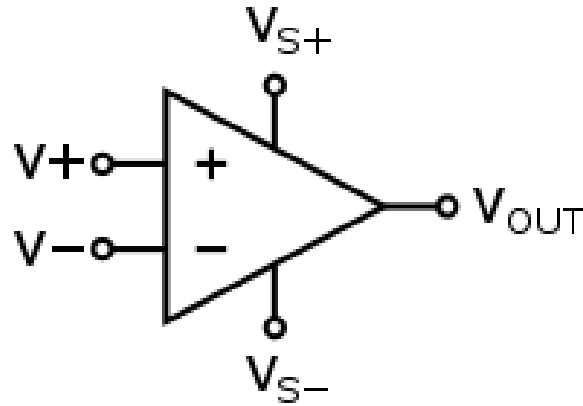


An operational amplifier (op amp) is an analog circuit block that takes a differential voltage input and produces a single-ended voltage output.

Inverting Op amp

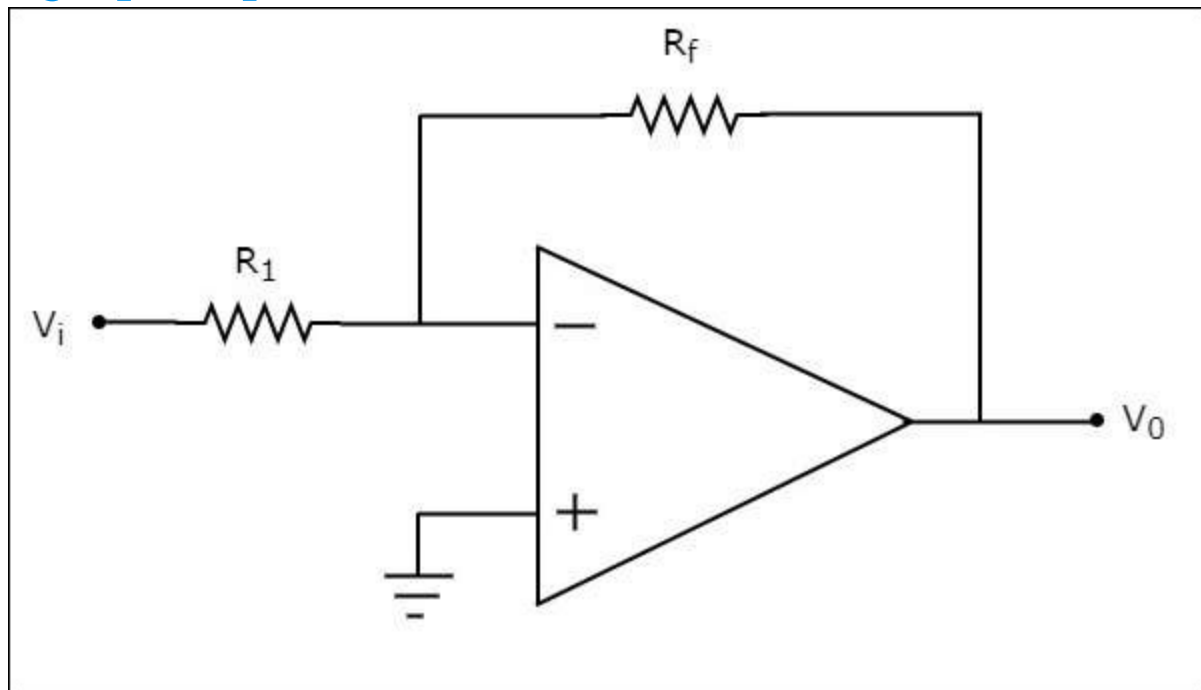


$$V_{out} = -\frac{R_f}{R_{in}} \times V_{in}$$

Non-inverting Op amp

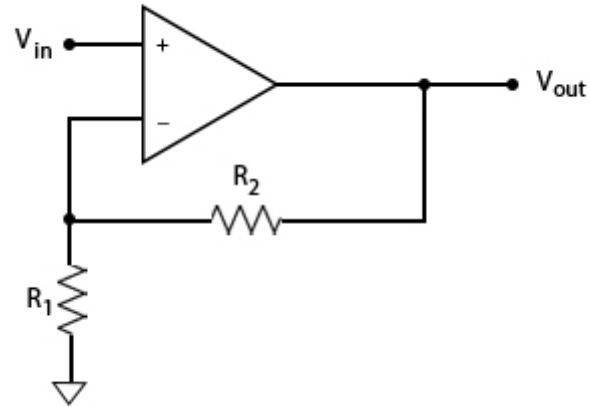

$$\Rightarrow v_o = v_i \left(1 + \frac{R_f}{R_1} \right)$$

Log Amplifier

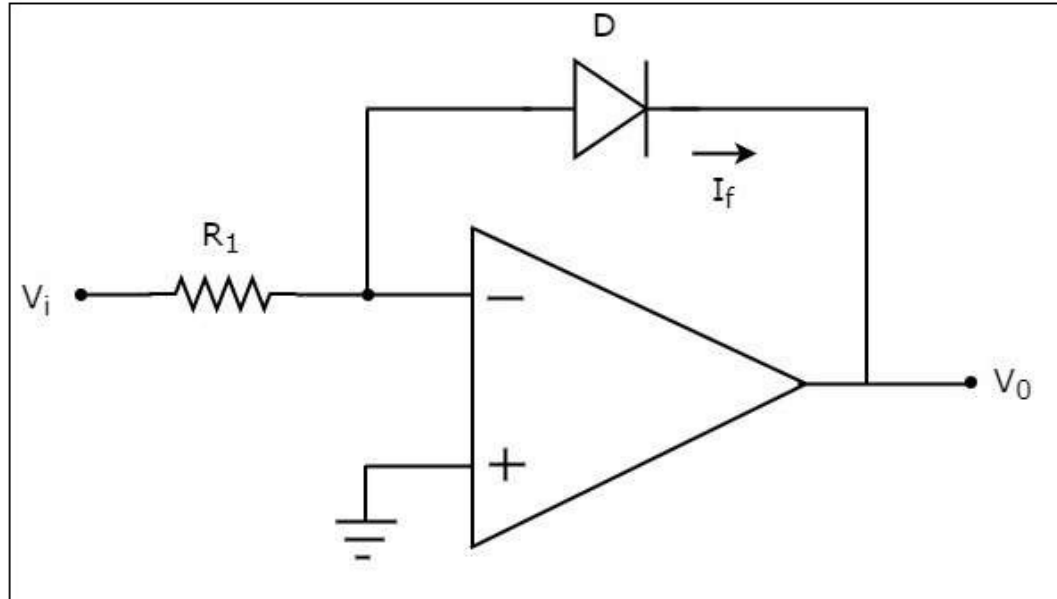

$$\log(xy) = \log(x) + \log(y)$$


A logarithmic amplifier, or a log amplifier, is an electronic circuit that produces an output that is proportional to the logarithm of the applied input.

Log Amplifier

The **nodal equation** at the inverting input terminal's node is –

$$\frac{0 - V_i}{R_1} + I_f = 0$$
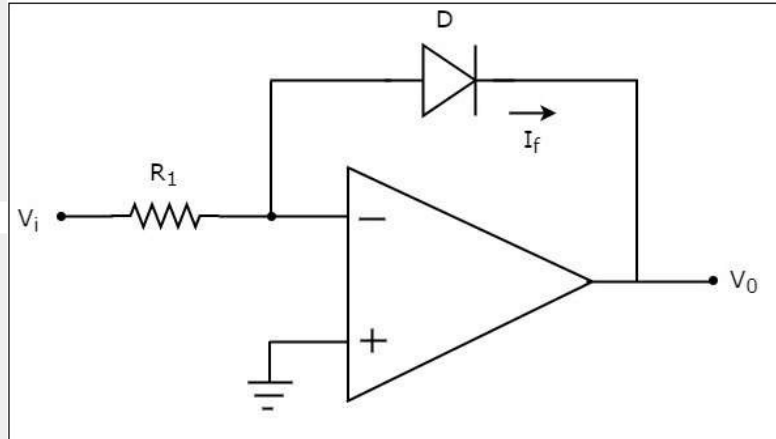
$$\Rightarrow I_f = \frac{V_i}{R_1} \dots \dots \text{Equation 1}$$



The following is the **equation for current** flowing through a diode, when it is in forward bias –

$$I_f = I_s e^{\left(\frac{V_f}{nV_T}\right)} \dots \dots \text{Equation 2}$$

Log Amplifier


The **KVL equation** around the feedback loop of the op amp will be –

$$0 - V_f - V_0 = 0$$

$$\Rightarrow V_f = -V_0$$

Substituting the value of V_f in Equation 2, we get –
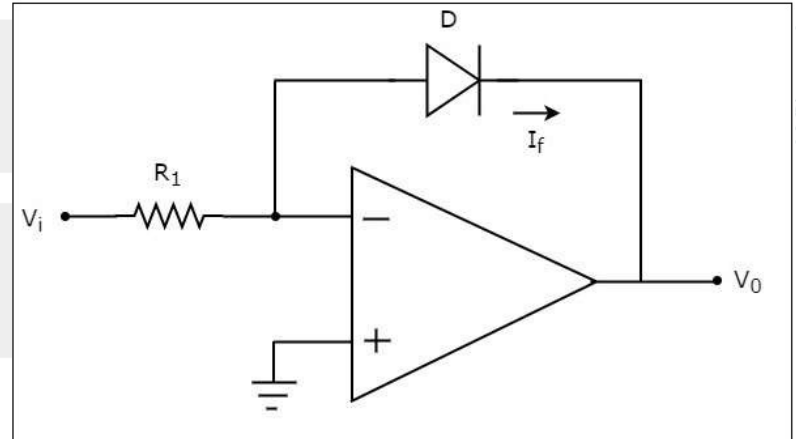
$$I_f = I_s e^{\left(\frac{-V_0}{nV_T}\right)} \dots\dots \text{Equation 3}$$




$$\frac{V_i}{R_1} = I_s e^{\left(\frac{-V_0}{nV_T}\right)}$$

$$\frac{V_i}{R_1 I_s} = e^{\left(\frac{-V_0}{nV_T}\right)}$$


Applying **natural logarithm** on both sides, we get –

$$\ln\left(\frac{V_i}{R_1 I_s}\right) = \frac{-V_0}{nV_T}$$
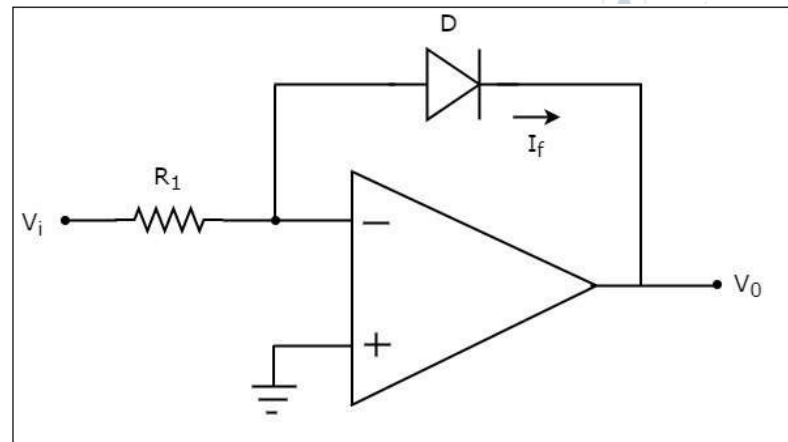
$$V_0 = -nV_T \ln\left(\frac{V_i}{R_1 I_s}\right)$$



AntiLog Amplifier

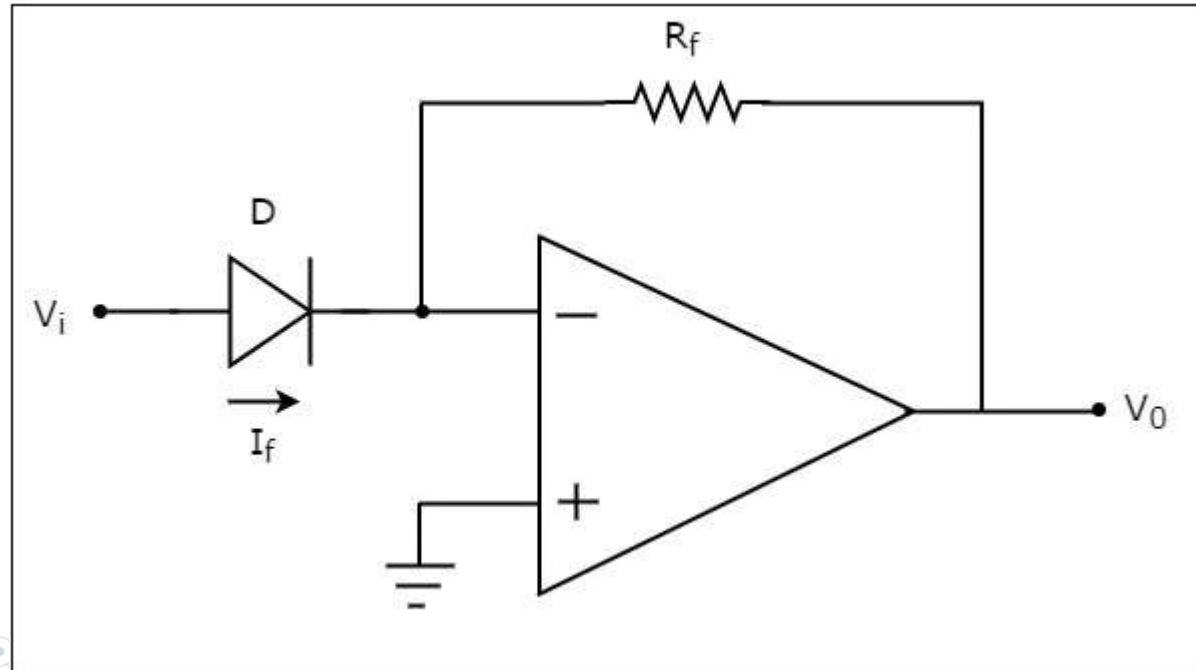


AntiLog Amplifier

The **nodal equation** at the inverting input terminal's node is –

$$-I_f + \frac{0 - V_0}{R_f} = 0$$

$$\Rightarrow -\frac{V_0}{R_f} = I_f$$
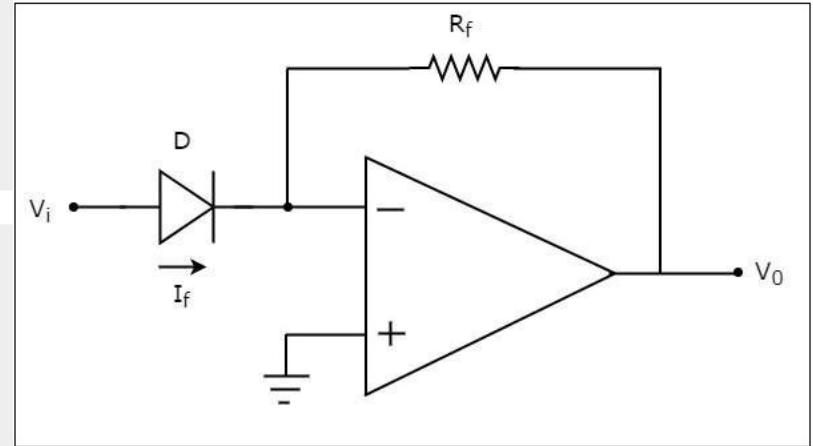
$$\Rightarrow V_0 = -R_f I_f \dots \dots \dots \text{Equation 4}$$




We know that the equation for the current flowing through a diode, when it is in forward bias, is as given below –

$$I_f = I_s e^{\left(\frac{V_f}{nV_T}\right)}$$

Substituting the value of I_f in Equation 4, we get

$$V_0 = -R_f \left\{ I_s e^{\left(\frac{V_f}{nV_T}\right)} \right\}$$

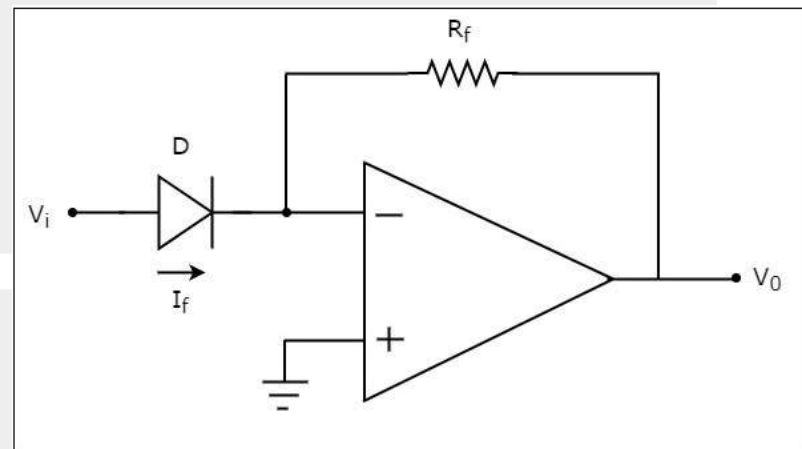
$$V_0 = -R_f I_s e^{\left(\frac{V_f}{nV_T}\right)} \dots\dots \text{Equation 5}$$



The KVL equation at the input side of the inverting terminal of the op amp will be

$$V_i - V_f = 0$$


$$V_f = V_i$$

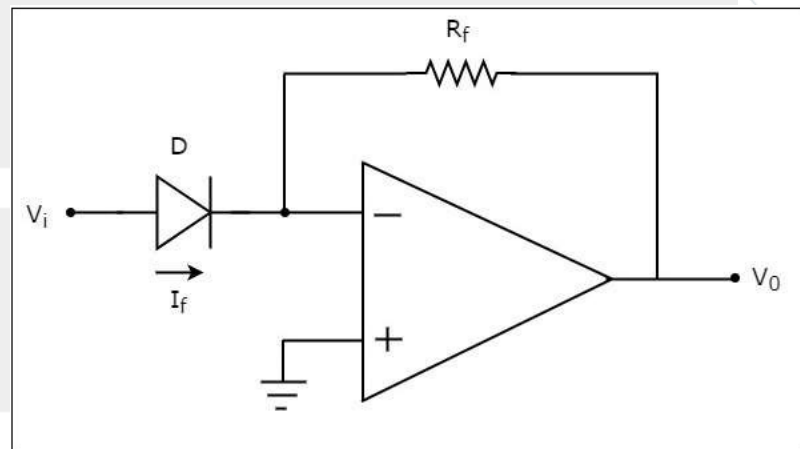

Substituting, the value of V_f in the Equation 5, we get –

$$V_0 = -R_f I_s e^{\left(\frac{V_i}{nV_T}\right)}$$

OPamp as Summer

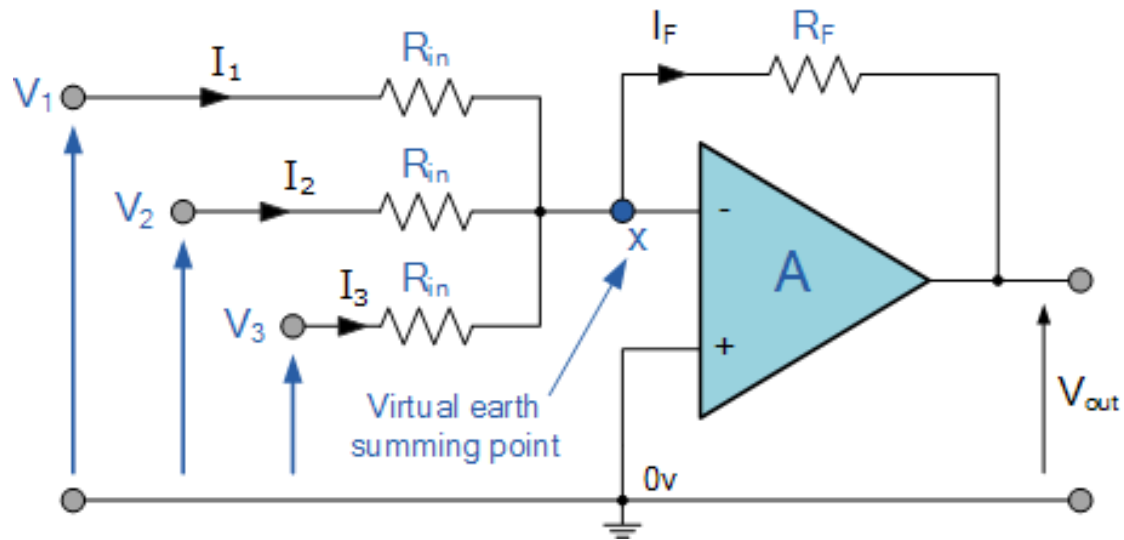


OPamp as Summer


$$I_F = I_1 + I_2 + I_3 = - \left[\frac{V_1}{R_{in}} + \frac{V_2}{R_{in}} + \frac{V_3}{R_{in}} \right]$$

Inverting Equation: $V_{out} = -\frac{R_F}{R_{in}} \times V_{in}$

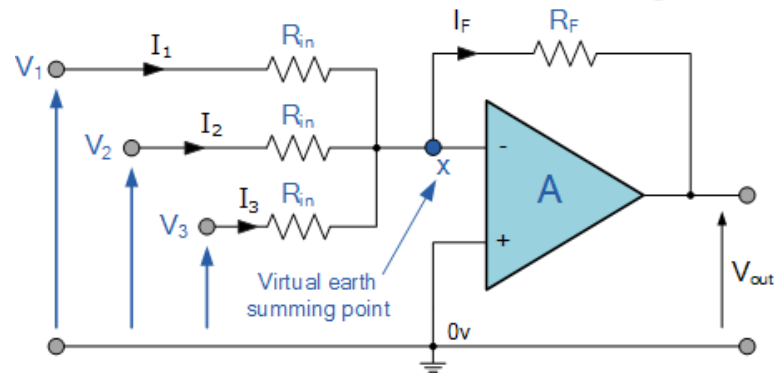then, $-V_{out} = \left[\frac{R_F}{R_{in}} V_1 + \frac{R_F}{R_{in}} V_2 + \frac{R_F}{R_{in}} V_3 \right]$




OPamp as Summer

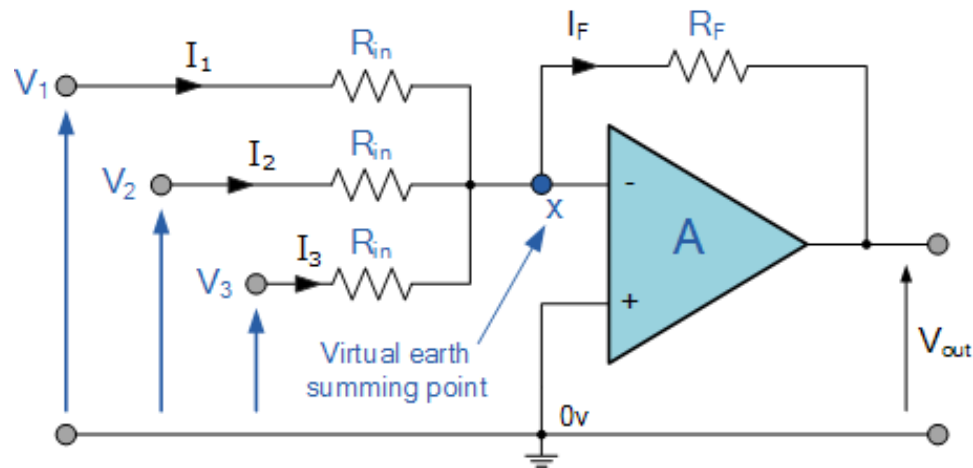


$$-V_{out} = \frac{R_F}{R_{IN}} (V_1 + V_2 + V_3 \dots \text{etc})$$

Multiplier

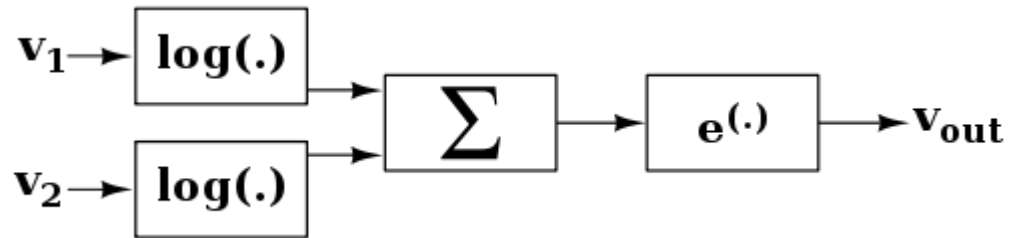


Multiplier Using Opamp

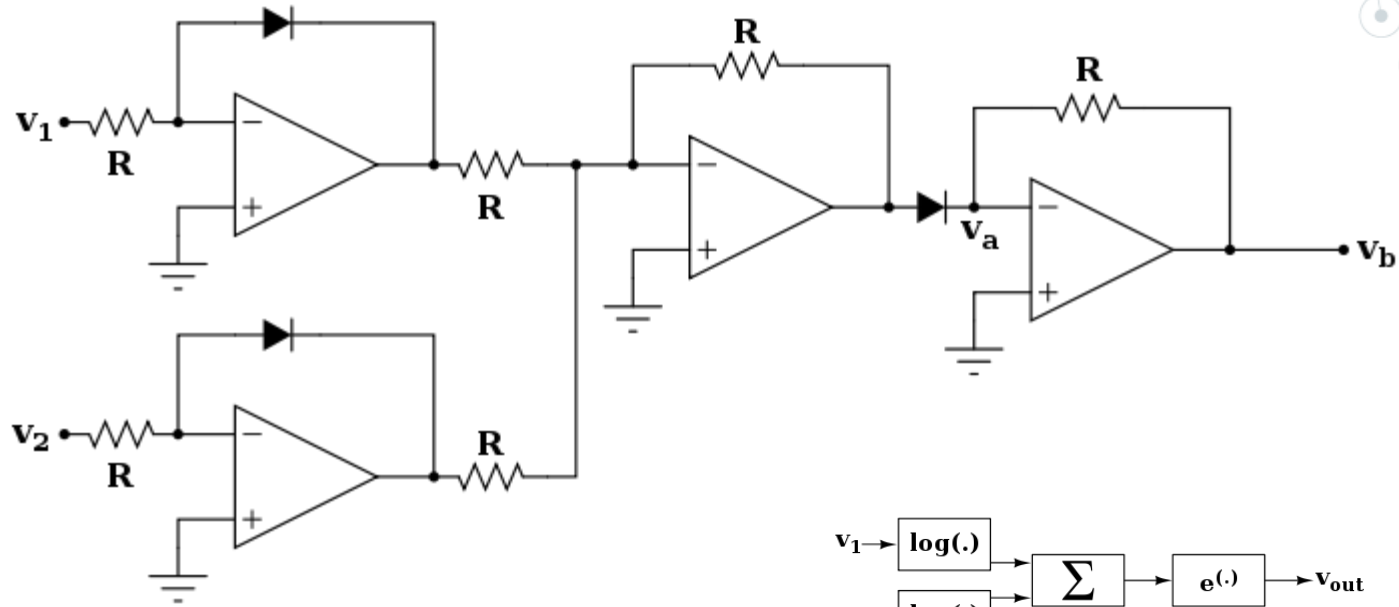

Generation of ASK




Generation of ASK signal

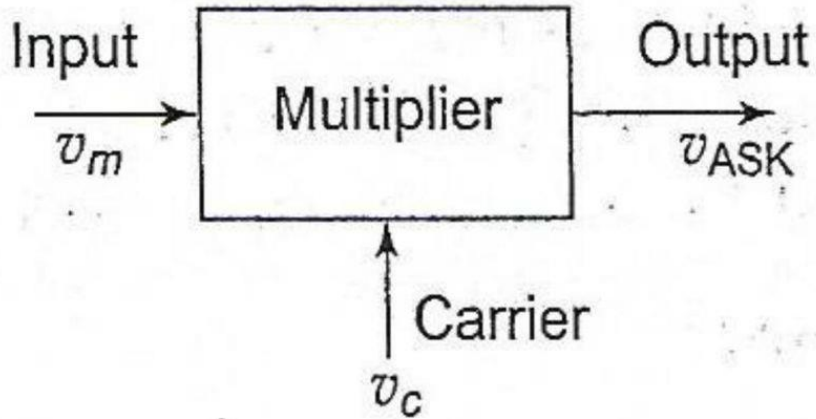

Block diagram of generation of ASK


Non-Coherent Detection of ASK

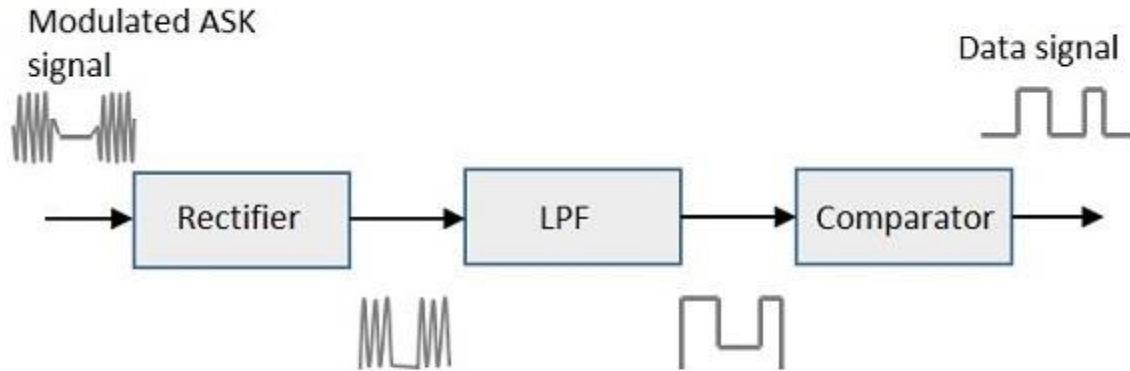


Asynchronous ASK detector

RF 433 Mhz Module

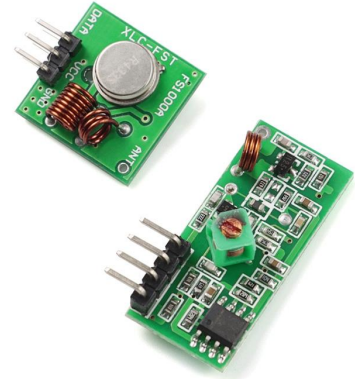
- Wireless (RF) Simplex Transmitter and Receiver
- Receiver Operating Voltage: 3V to 12V
- Receiver Operating current: 5.5mA
- Operating frequency: 433 MHz
- Transmission Distance: 3 meters (without antenna) to 100 meters (maximum)
- Modulating Technique: ASK (Amplitude shift keying)
- Data Transmission speed: 10Kbps
- Circuit type: Saw resonator



RF 433 Mhz Module

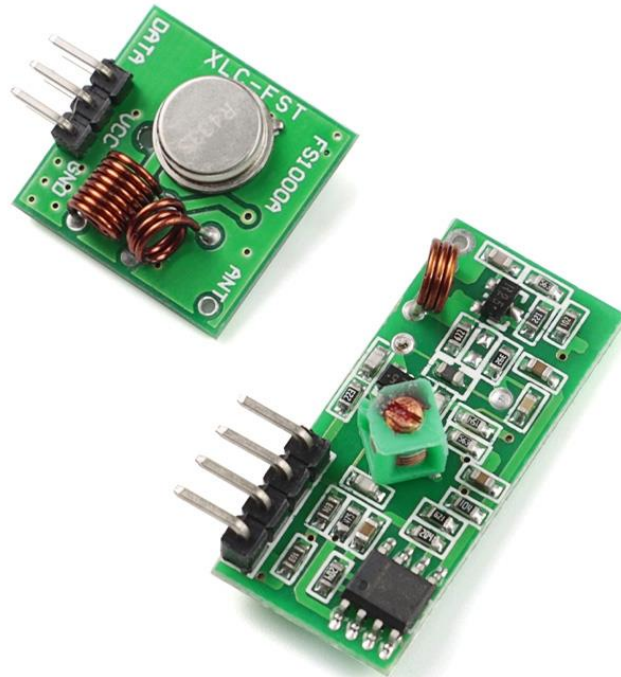


RF 433 Mhz Transmitter Pin Layout

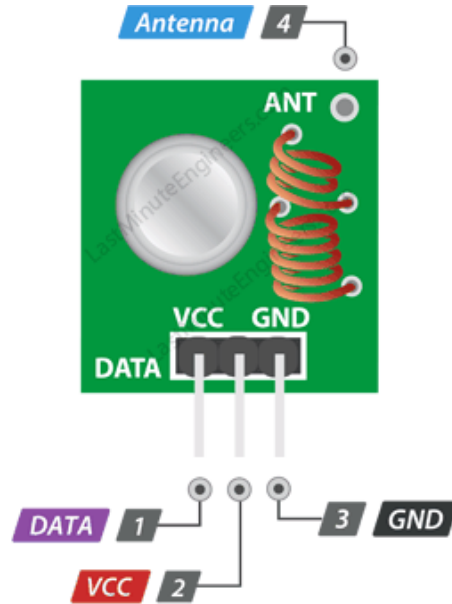


433MHz Tx Pinout

RF 433 Mhz Receiver Pin Layout

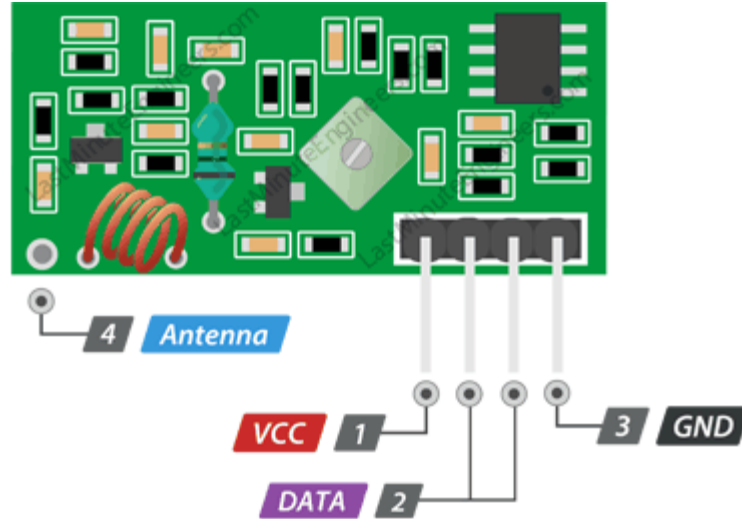


433MHz Rx Pinout

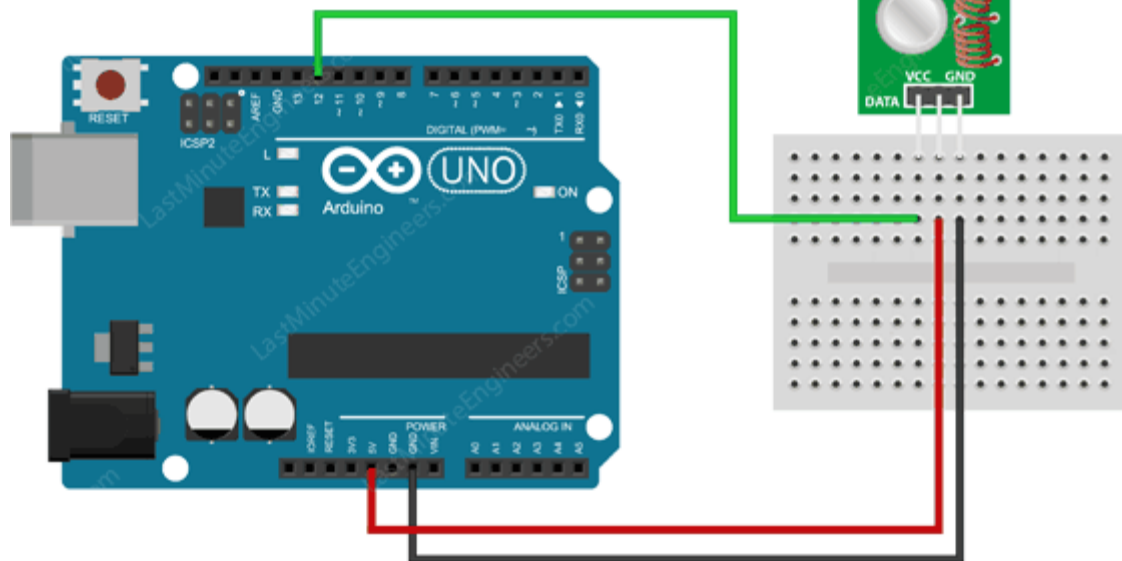





Last Minute
ENGINEERS.com

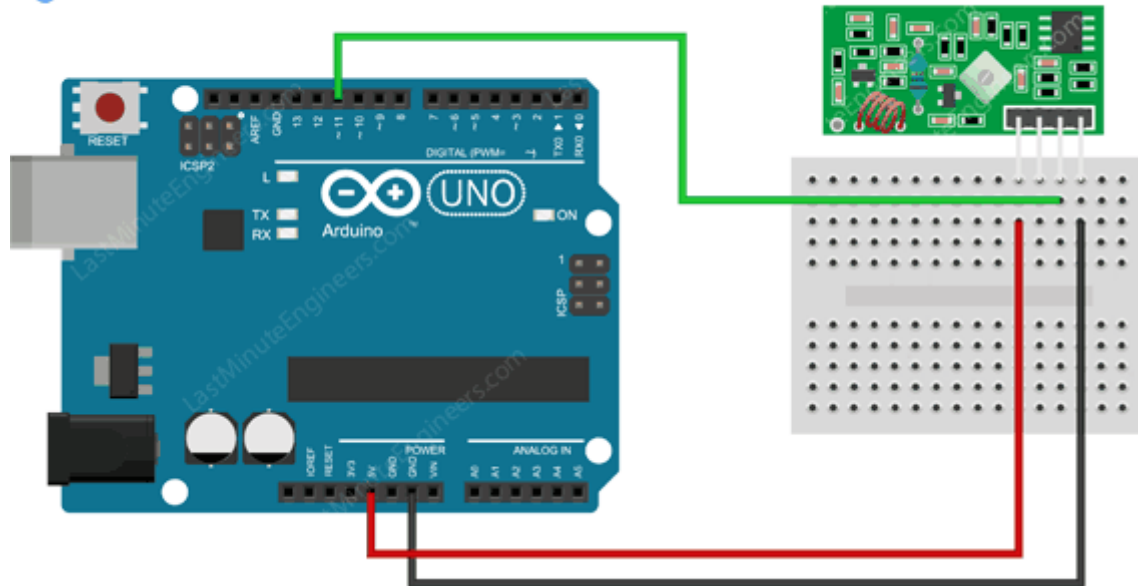

Marconi Antenna


-17.3 cm piece of solid wire

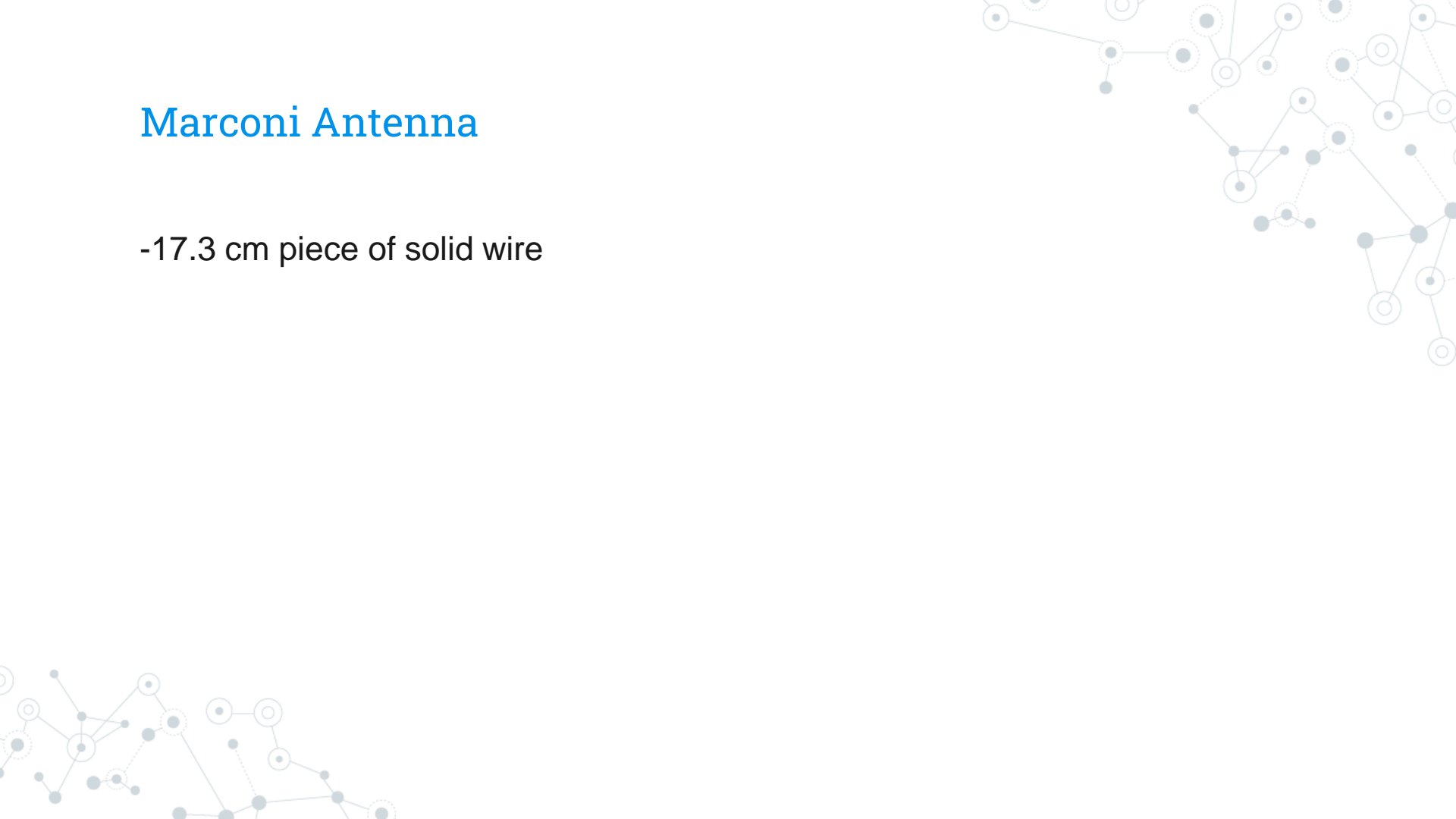

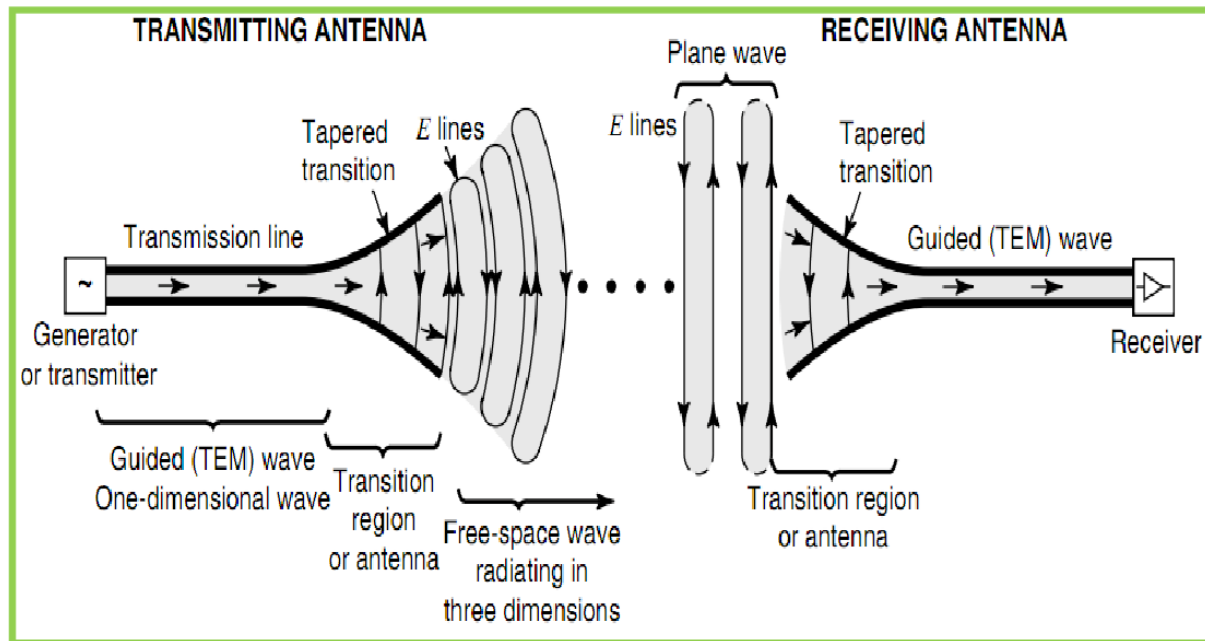



Marconi Antenna

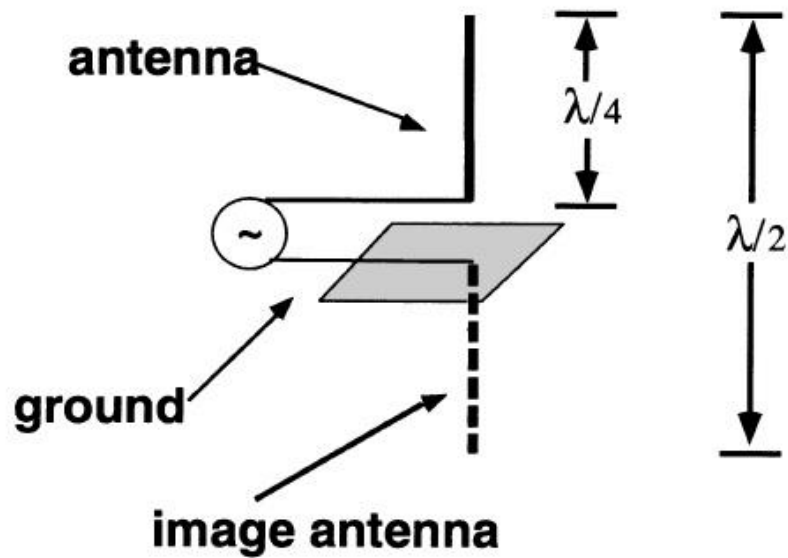

THANK YOU

